

# Electronics Laboratory

Winter semester 2025

---

## Lab 2 – Bipolars

Name \_\_\_\_\_ Reg. Nr. \_\_\_\_\_

Name \_\_\_\_\_ Reg. Nr. \_\_\_\_\_

Score and comments (only for tutors, please leave blank)

*Please fill out this cover sheet and submit it with your lab report.*



## 2 Lab 2 – Bipolars

### Introduction

We will begin by studying the operating behavior of a bipolar transistor, deriving the characteristics we have used in lecture by simulation and measurement. Once we understand our bipolar, we will then analyze a common-emitter amplifier, looking at the time and frequency response, and then consider a simple bipolar current source, deriving its operating limits.

### Notes

- You will need the SPICE directive `.step` to perform parameter sweeps in the simulation sections. It would be worth your while to refer to the LTSpice manual for a description of how to use this directive and how to define the parameter to be swept.



## 2.1 Preparation

Please answer the following questions *before* beginning with the simulations or experiments. Then complete the preparation quiz “Preparation 2.1 – Bipolars” on Ilias using your results. The points for this preparation section will only be awarded via Ilias.

### 2.1.1 Beta

Consider the circuit in Figure 2.2.1 below, where  $V_{DD} = 10\text{ V}$ ,  $R_B = 100\text{ k}\Omega$  and  $R_C = 200\text{ }\Omega$ . You apply  $V_i = 2\text{ V}$  and measure  $V_o = 9.16\text{ V}$  at the output. What is  $\beta$  for this transistor? Make standard assumptions.

### 2.1.2 Early voltage

The measurement of which parameters is typically used to determine the Early voltage?

### 2.1.3 Operating point

Below are given the output characteristics of a bipolar transistor employed in a simple common-emitter circuit, such as that of Figure 2.2.1.

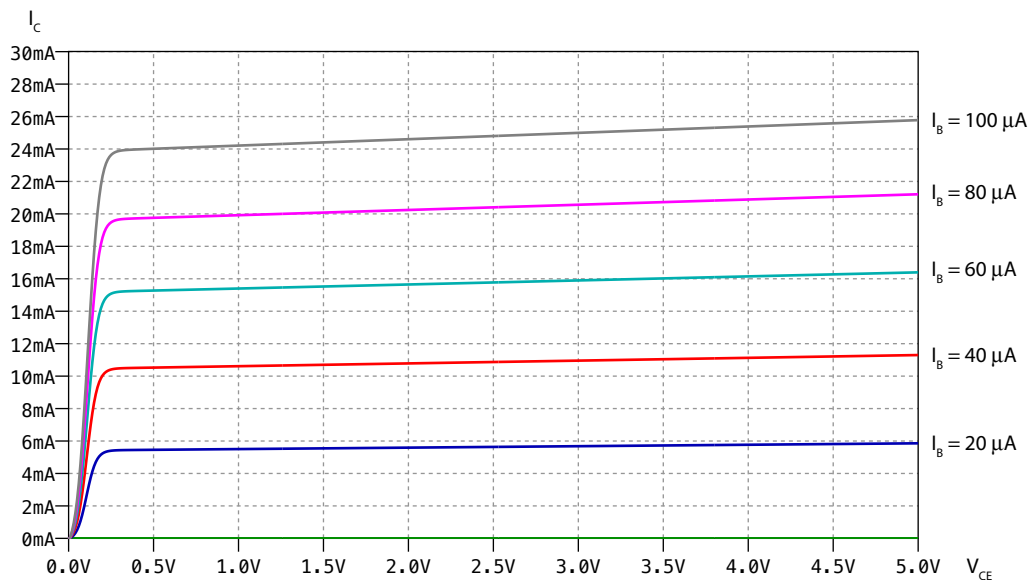


Figure 2.1.1

If  $V_{DD} = 5\text{ V}$  and  $R_C = 180\text{ }\Omega$  and you measure an output voltage of  $V_o = 3.0\text{ V}$ , what base current flows into the transistor?



#### 2.1.4 Small signal model

For the operating point you determined in Question 2.1.3, calculate the value for the differential input resistance,  $r_\pi$ . Assume room temperature.

#### 2.1.5 Temperature effects

If the temperature of the transistor increases, would you expect any change in the value for  $r_\pi$ ?

#### 2.1.6 Amplification

Consider the CE amplifier in Figure 2.3.1 below, which uses the bipolar transistor whose output characteristics are shown in Figure 2.1.1. Take  $R_o = 0$ ,  $R_C = 680\ \Omega$  and  $V_{DD} = 10\text{ V}$ . If your bias network generates  $I_B = 40\ \mu\text{A}$ , calculate the small-signal voltage gain  $A_V = v_o/v_i$ .

#### 2.1.7 Current source

What are the relationships between currents and voltages in a current source?



## 2.2 Bipolar characteristics

We will simulate and experimentally characterize a bipolar transistor using a simple common-emitter configuration.

### 2.2.1 Simulation

Consider the common-emitter circuit shown in Figure 2.2.1.

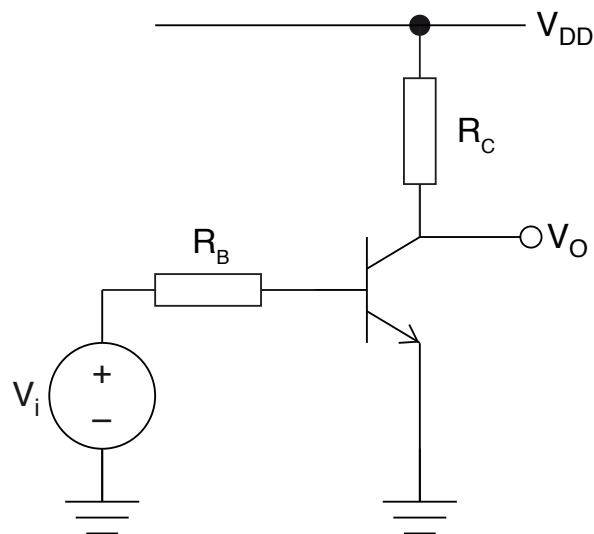


Figure 2.2.1

- Set up a SPICE simulation of this circuit using a BC547B bipolar and setting  $R_B = 100\text{ k}\Omega$  and  $R_C = 200\text{ }\Omega$ .
- Set  $V_{DD} = 10\text{ V}$  and apply a ramp for  $V_i$  of  $0\text{ V}$  to  $10\text{ V}$  (use the `.dc` directive).
- During the ramp, measure  $I_B$ ,  $I_C$  as well as  $V_{BE}$ .
- Determine  $\beta$  for this transistor at low currents.
- Plot  $I_B$  as a function of  $V_{BE}$ .
- Plot  $I_C$  and  $\beta$  as a function of  $I_B$  on a single graph. Is  $\beta$  constant? Comment on this.
- Now, again using the SPICE directive `.dc`, set a ramp for  $V_{DD}$  from  $0\text{ V}$  to  $10\text{ V}$  while stepping  $V_i$  from  $0\text{ V}$  to  $5\text{ V}$  in  $1\text{ V}$  steps.
- Record and plot  $I_C$  as a function of  $V_{CE}$  for the different  $I_B$ , not forgetting to properly label your plot with the  $I_B$  values.
- Determine the Early voltage for each  $I_C/V_{CE}$  trace; how do the values compare?



### 2.2.2 Measurement

In the “BIPOLAR” section of the electronics board, we will use the *BJT characteristics* circuit, shown in Figure 2.2.2.

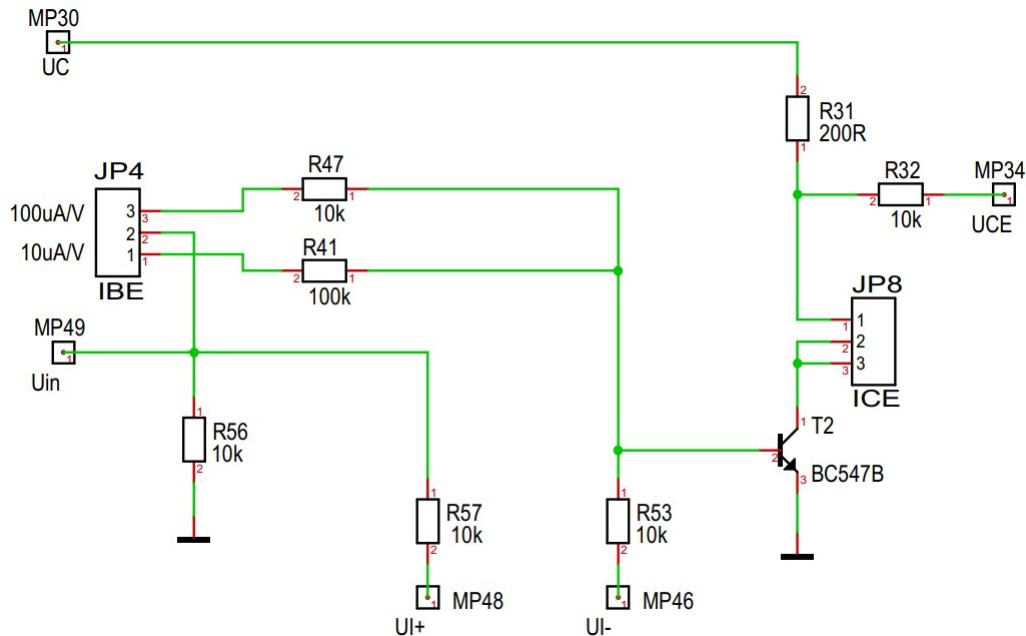


Figure 2.2.2: Schematic of the *BJT characteristics* circuit

We will undertake three measurements: the  $I_B/V_{BE}$  characteristic (a – g); the current gain  $\beta$  (h – o); and the  $I_C/V_{CE}$  characteristic (p – w).

#### $I_B/V_{BE}$ characteristic

- Short-circuit pins 1 and 2 of the jumper *JP8*.
- Connect  $R_{41}$  via jumper *JP4*.
- Connect the two measurement points *MP48* and *MP46* to the differential amplifier and use this to measure the voltage drop across  $R_{41}$  (the current  $I_B$  can be calculated based on this voltage).
- Set the measurement point *MP30* ( $V_{DD}$ ) to 10 V and measure the applied voltage to verify the value.
- Apply a voltage ramp (Triangle, 0 V  $\rightarrow$  5 V, 50 %, 50 Hz) to the measurement point *MP49*. Set a proper offset and amplitude to have a well-defined triangle input voltage.
- Measure  $V_{BE}$  directly at the measurement point *MP46*.
- Measure and plot  $I_B$  as a function of  $V_{BE}$ . Save your data.

### Current gain

- (h) Connect the handheld multimeter to measure the current  $I_C$  between pins 1 and 2 of the jumper  $JP8$ .
- (i) Again connect  $R_{41}$  via jumper  $JP4$ .
- (j) Again connect the two measurement points  $MP48$  and  $MP46$  to the differential amplifier to measure the voltage drop across  $R_{41}$ .
- (k) Set the measurement point  $MP30$  ( $V_{DD}$ ) to 5 V and measure the applied voltage.
- (l) Apply a dc voltage at measurement point  $MP49$ , increasing in value stepwise from 0 V to 2 V in 0.1 V steps, thereby increasing  $I_B$ . Tune your input voltage using the *Waveforms* software until you measure the defined voltage. This procedure applies to any DC input voltage from the signal generator.
- (m) Measure  $I_C$  as a function of  $I_B$ .
- (n) Calculate  $\beta$  as a function of  $I_B$ .
- (o) Plot  $I_C$  and  $\beta$  as a function of  $I_B$  on a single diagram.

### $I_C/V_{CE}$ characteristic

- (p) Short-circuit *pin 1* and *pin 2* of the jumper  $JP8$ .
- (q) Again connect  $R_{41}$  via jumper  $JP4$ .
- (r) Connect the measurement point  $MP30$  and pin 3 of the jumper  $JP8$  to the differential amplifier to measure the voltage drop across  $R_{31}$  (you can calculate the current  $I_C$  based on this value).
- (s) Apply a voltage ramp (Triangle, 0 V  $\rightarrow$  10 V, 50 %, 50 Hz) to the measurement point  $MP30$  ( $V_{DD}$ ).
- (t) Apply a dc voltage at measurement point  $MP49$ , increasing in value stepwise from 0 V to 2 V in 0.5 V steps, thereby increasing  $I_B$ .
- (u) Measure  $V_{CE}$  directly at the measurement point  $MP34$ .
- (v) Measure and plot  $I_C$  versus  $V_{CE}$  for the different  $I_B$  values. Use your results from the previous experiment for the labeling of  $I_B$ .
- (w) Determine the Early voltage for each trace and compare the values.



## 2.3 Common emitter amplifier

Based on the bipolar we characterized in the first section, we will now simulate and experimentally characterize a bipolar common-emitter amplifier.

### 2.3.1 Simulation

Consider the common-emitter amplifier shown in Figure 2.3.1. We will model the amplifier twice, once in time domain and once in the frequency domain, and compare the results.

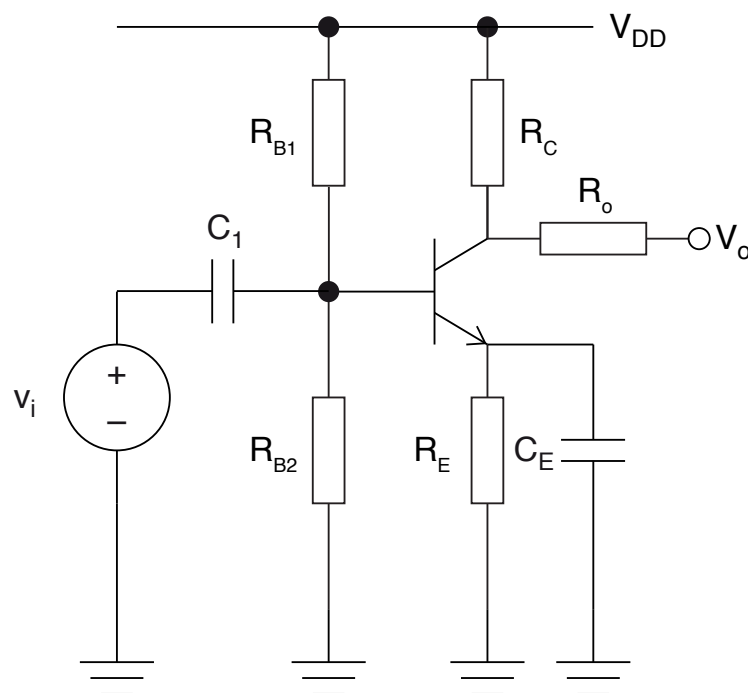


Figure 2.3.1

- Set up a SPICE implementation of the circuit in Figure 2.3.1, using the following component values found on the electronics board:  $R_{35}$ ,  $R_{42}$ ,  $R_{37}$ ,  $R_{52}$ ,  $C_{14}$ , and  $C_{16}$  (see Figure 2.3.2 below). The transistor model is already included in LTSpice.
- For  $R_E$ , set a parameter sweep between the values of  $R_{48}$  and  $R_{51}$  using the `.step` directive.
- Use a supply voltage of  $V_{DD}(=V_{MP38}) = 10\text{ V}$ .
- Add an RC high pass filter to the output after  $R_{52}(=R_o)$  with  $C_{HP} = 120\text{ }\mu\text{F}$  and  $R_{HP} = 10\text{ k}\Omega$ . From there, measure the output signal  $V_o$ .
- For the time domain simulation, set the input signal  $V_i$  as a sine wave with an amplitude of  $15\text{ mV}$  and a frequency of  $10\text{ kHz}$ .





- (f) Using the `.tran` directive, record the input and output signals for this circuit over 500  $\mu$ s. From your data, determine the gain (in dB) and phase shift between input and output for both emitter resistor values.
- (g) For the frequency domain simulation, replace the `.tran` directive with `.ac`, defining a frequency range from 1 kHz to 100 MHz. Plot both amplitude and phase, again for both emitter resistor values.
- (h) Compare the four simulation results for gain and phase shift for a frequency of 10 kHz.

### 2.3.2 Measurement

In the “BIPOLAR” section of the electronics board, we will use the *BJT amplifier* circuit, shown in Figure 2.3.2.

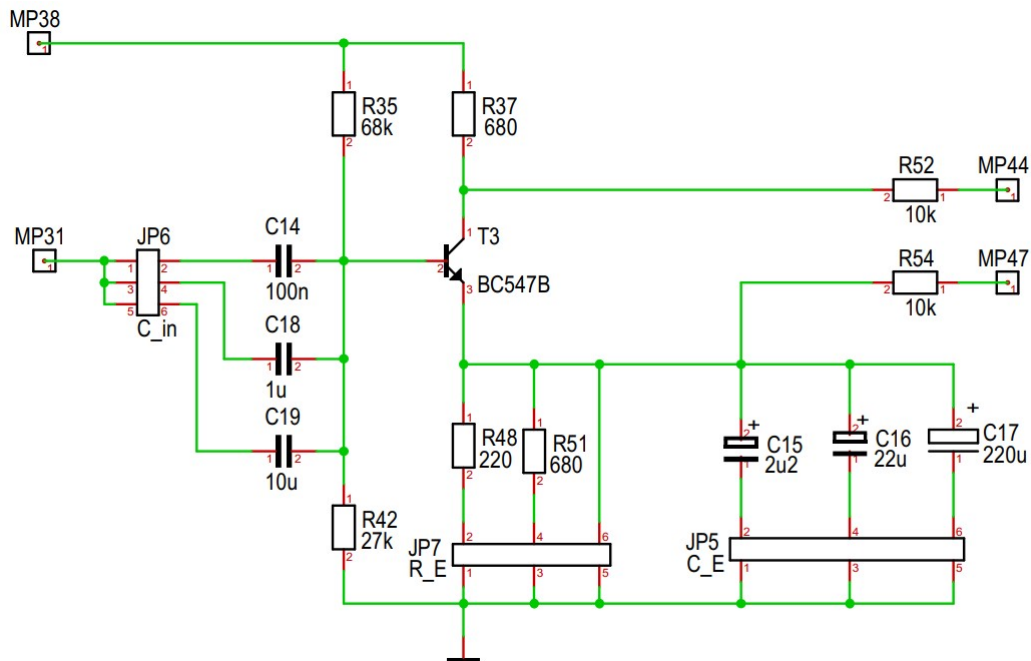


Figure 2.3.2: Schematic of the *BJT amplifier* circuit

- (a) Configure the amplifier using *C14*, *C16* and *R48*.
- (b) Set the measurement point *MP38* to 10 V and measure the actual applied voltage.
- (c) Measure the output via the measurement point *MP44*. Set the switch on the oscilloscope to *AC* to add a high-pass filter to the input and thereby filter out the offset.
- (d) Apply a sine wave (Sine,  $\pm 15$  mV, 50 %, 10 kHz) to the measurement point *MP31* and measure it directly (switch the oscilloscope to *AC*).

- (e) Measure the input and output characteristics; save your data.
- (f) Measure the time offset of both signals by means of two X-cursors and calculate the phase shift from these values.
- (g) Let WaveForms display the phase difference of both signals (*Waveforms / Scope / Measurements / Add / Custom Global / Add*). The default setting calculates phase difference.
- (h) Using your measured characteristics, calculate the gain (in dB) for the given system.
- (i) Perform a spectral analysis. To do this, open the *Spectrum* menu in *WaveForms*. Make a *Single* recording of both inputs. Measure both peaks at 10 kHz using an X-cursor. From this, calculate the gain (in dB).
- (j) Now perform a small signal analysis. To do this, open the *Network* menu in *WaveForms*. In the header, set the frequencies from 1 Hz to 100 kHz (at 16 samples). Set 15 mV as amplitude on the right. Perform a *single* recording of the output signal.
- (k) From this measurement, determine the gain (in dB) and phase shift at 10 kHz and compare with your spectral analysis and simulation results.
- (l) Repeat the tasks a – k using the emitter resistor  $R_{51}$ .
- (m) Plot the small signal analysis characteristics (gain in dB and phase) of both emitter resistors in a single plot.



## 2.4 Current source

We will now analyze, design and characterize a bipolar-based current source.

### 2.4.1 Simulation

Consider the simple bipolar current source configuration shown in Figure 2.4.1.

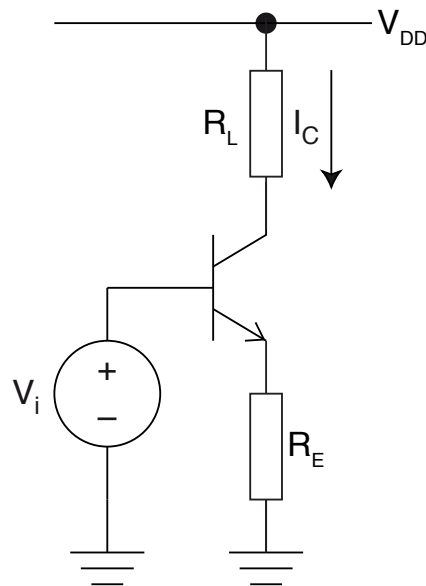


Figure 2.4.1

- Set up a SPICE simulation of this circuit using the bipolar transistor  $T_4$  employed on the electronics board.
- Set  $V_{DD} = 10\text{ V}$ .
- Add the SPICE directive `.op`.
- Perform a parameter sweep for the load resistor  $R_L$  (again using the `.step` directive) from  $1\text{ }\mu\Omega$  to  $10\text{ k}\Omega$  with ten sample points per decade.
- Run the simulation for input voltages  $V_{in1} = 2.5\text{ V}$  and  $V_{in2} = 5\text{ V}$  and emitter resistances  $R_{E1} = 100\text{ }\Omega$  and  $R_{E2} = 200\text{ }\Omega$  (thus four simulations).
- Measure and plot  $I_C$  as a function of  $R_L$  for all combinations of  $V_{in}$  and  $R_E$  in a graph with a logarithmic abscissa.
- Determine the maximum current  $I_{C(max)}$  of the current source for each case.
- Also determine in each case the maximum load ( $R_{L(max)}$ ) at a maximum deviation of 5% from  $I_{C(max)}$ .



- (i) Analyze and interpret any linear or non-linear characteristics which you determine for all parameters.

### 2.4.2 Measurement

In the “BIPOLAR” section of the electronics board, we will use the *BJT current source* circuit, shown in Figure 2.4.2, as well as the *diode characteristics* circuit (Figure 2.4.3) and *LED characteristics* circuit (Figure 2.4.4) from the “DIODES” section.

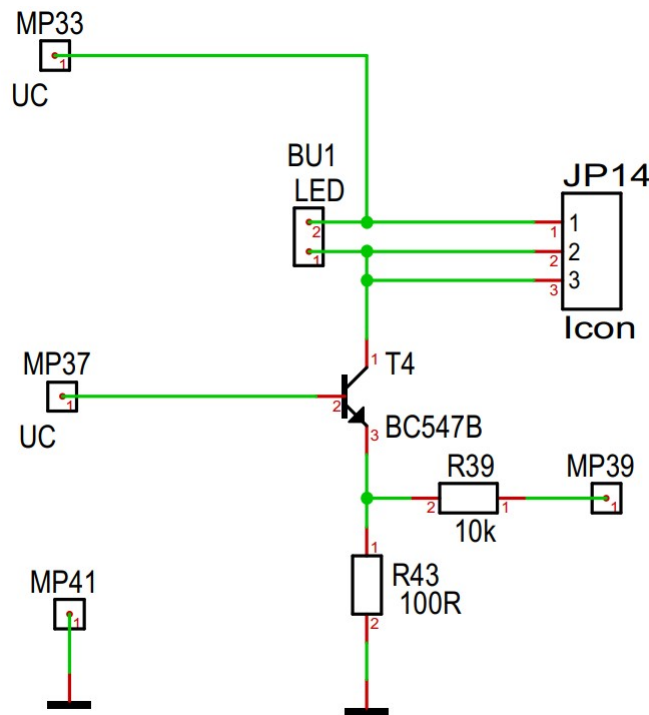


Figure 2.4.2: Schematic of the *BJT current source* circuit

- Set the measurement point *MP33* to 10 V and measure the actual applied voltage.
- Connect the handheld multimeter to measure the current between *pin 1* and *pin 2* of the jumper *JP14*.
- Successively connect DC voltages of  $V_{in1} = 2.5\text{ V}$  and then  $V_{in2} = 5\text{ V}$  to the measurement point *MP37*.
- Measure the current  $I_C$  as a function of the input voltage; save your data.
- Now connect the handheld multimeter to measure the current between *Pin 1* of the jumper *JP14* and *MP23*. Also connect *Pin 3* of the jumper *JP14* to *MP26*.
- Connect a DC voltage of  $V_{in3} = 3.9\text{ V}$  to the measurement point *MP37*.



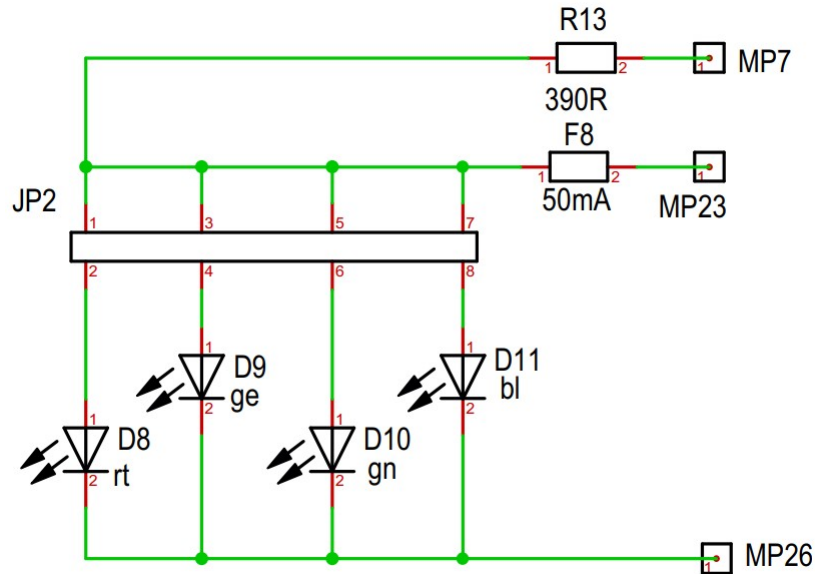


Figure 2.4.3: Schematic of the *diode characteristics* circuit

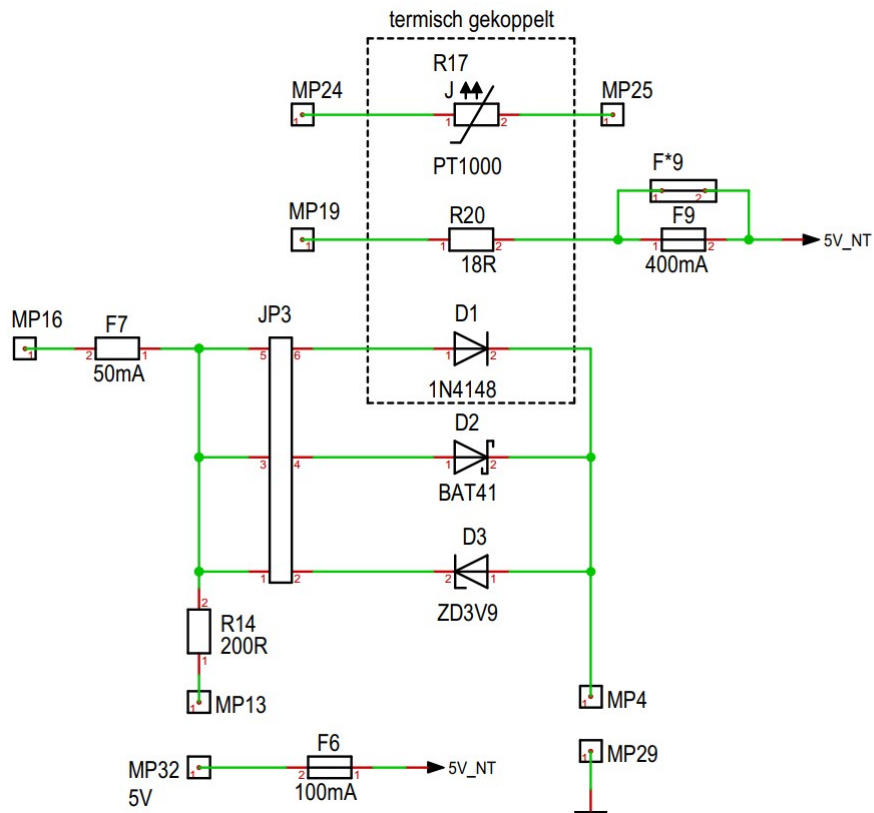


Figure 2.4.4: Schematic of the *LED characteristics* circuit

- (g) Connect all the LEDs one at a time to the current source using jumper *JP2* and determine  $I_C$  in each case. Observe the light-emission behavior of the LEDs and

note down your (subjective) observations.

- (h) Remove the input voltage from  $MP37$ . In its place, connect  $MP13$  to  $MP33$ ,  $MP16$  to  $MP37$  and  $MP4$  to  $GND$ . Also connect the Z-diode to the current source using jumper  $JP3$ .
- (i) Again connect all the LEDs one at a time to the current source using jumper  $JP2$  and determine  $I_C$  in each case. Again observe the light-emission behavior of the LEDs and note down your (subjective) observations.

